



# Programmable logic circuits (ex. PLD)

## Exercises embedded systems

### 1 Programmable Logic Device (PLD)

#### 1.1 Exclusive OR function in a PAL

Draw the fuses in the scheme of the following figure to generate the functions  $out1 \leftarrow in1 \text{ xor } in2$ ; and  $out2 \leftarrow in2 \text{ xor } in3 \text{ xor } in4$ .

 


Figure 1: PAL4H2

Determine the number of necessary inputs of the OR gate to calculate the parity for an 8-bit word.

#### 1.2 Counter in a PAL

Draw the fuses in the scheme of the following figure to create a 2-bit counter. The input  $in1$  serves as an "enable" control: when  $in1 = '0'$  the counter is stopped and when  $in1 = '1'$  then it counts.

 


Figure 2: PAL4R2

Set the number of necessary inputs of the OR gate to create an 8-bit counter.

## 2 Complex Programmable Logic Device (CPLD)

### 2.1 Number comparison

For two numbers coded on 8 bits, determine the number of necessary inputs of the OR gate in a CPLD to make the following comparisons:

In a circuit, you need to determine if a regularly incrementing counter overflows a value stored in a register. Find a way to make this circuit as small as possible.

## 3 Field Programmable Gate Array (FPGA)

### 3.1 Multiplexer

Estimate the number of 8-input OR gates needed to create a multiplexer from 16 to 1.

Estimate the number of 4-input logic blocks needed to create the same multiplexer.

### 3.2 Counter

Based on the basic circuit of a FPGAs, as shown in the following figure, draw the scheme of a 6-bit counter, which counts continuously (without "Enable" control).

 


Figure 3: Base logic block of a [FPGA](#)

From this diagram, determine the number of basic blocks used to implement a 16-bit counter.

## Acronyms

**CPLD** Complex Programmable Logic Device. [2](#)

**FPGA** Field Programmable Gate Array. [2](#), [3](#)

**PLD** Programmable Logic Device. [1–3](#)